

Digital Logic

Tutorial:4 (Simplification & Combinational Logic)

Dead line: 2080/11/02

- 1) State De Morgan's theorem and verify it using venn diagram.
- 2) Using K-map, simplify the following Boolean functions in SOP and POS form:
 - i) $F(A,B,C,D)=\sum(5,7,9,12,13,14,15)$ with don't care $d(A,B,C,D)=\sum(3,6,8)$.
 - ii) $F(A,B,C,D)=\sum(0,6,8,13,14)$ with don't care $d(A,B,C,D)=\sum(2,4,10)$.
 - iii) $F(A,B,C,D)=\sum(2,3,7,10,11,14)$ with don't care $d(A,B,C,D)=\sum(1,5,15)$.
 - iv) $F(A,B,C,D)=\sum(1,4,5,6,12,14,15)$ with don't care $d(A,B,C,D)=\sum(10,11)$.

Implement i) & II) using NAND gate only and iii) & iv) using NOR gate only. Use 2-input gates only.

- 3) Simplify $F(w,x,y,z)=\sum(2,3,4,5,6,7,11,14,15)$ in POS form and implement with OR & AND gates.
- 4) Draw X-OR gate with minimum number of NAND gates. Also show that dual of X-OR is its complement.
- 5) Design a full subtractor circuit. Also construct it using two half subtractors.
- 6) Draw the truthtable of a full adder. Show that a full adder can be implemented using two half adders and an OR gate.
- 7) Design a combinational circuit with 4-input lines that represents a decimal digits in BCD and 4-output lines that generates the 9's complement of the input digits.
- 8) Design a combinational circuit that converts a decimal digit from 8 4 -2 -1 to the BCD.
- 9) Design a combinational circuit that converts 4-bit reflected code number to 4-bit binary number. Implement the circuit with X-OR gates.
- 10) Design a combinational circuit to generate odd parity of 3-bits. Also design a combinational circuit to check for odd parity. A logic-1 is required when the 4-bits donot constitute an odd parity.
- 11) Simplify the Boolean function:
 $F=A'B'D'+A'CD+A'BC$ with don't care $D=A'BC'D+ACD+AB'D'$. Implement it using
 - i) NAND gates only
 - ii) NOR gates only {Use 2-i/p gates only for both the cases}
- 12) Show that $(A \oplus B \oplus C \oplus D) = \sum(0,3,5,6,9,10,12,15)$.
- 13) Design a combinational logic circuit which converts BCD to seven segment decoder. Use the proper don't care conditions.